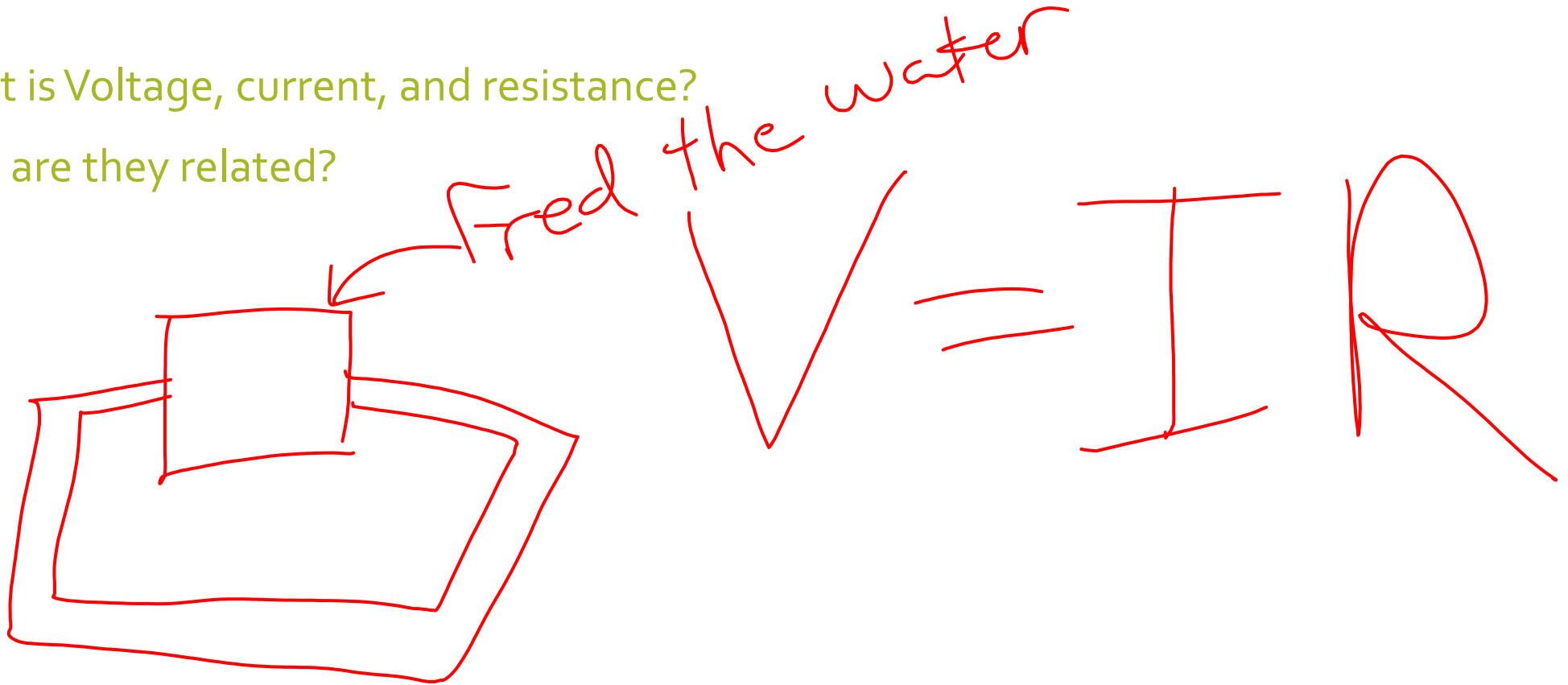


# SERIES AND PARALLEL CIRCUITS

---


# Opening

- What is Voltage, current, and resistance?
- How are they related?





# Simplifying a series circuit

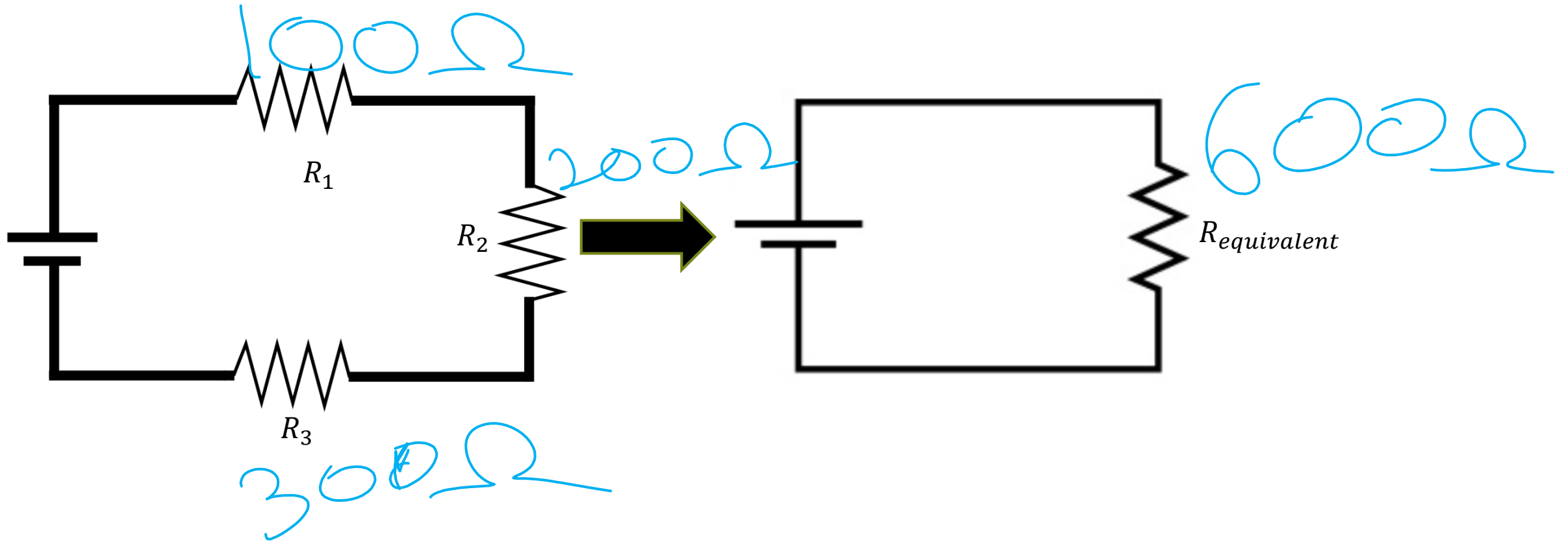

# Parallel Circuits

Voltage: All the same


$$V_{total} = V_1 = V_2$$

Current: Divided between each "branch"


$$I_{total} = I_1 + I_2$$

Resistance: reduces total resistance
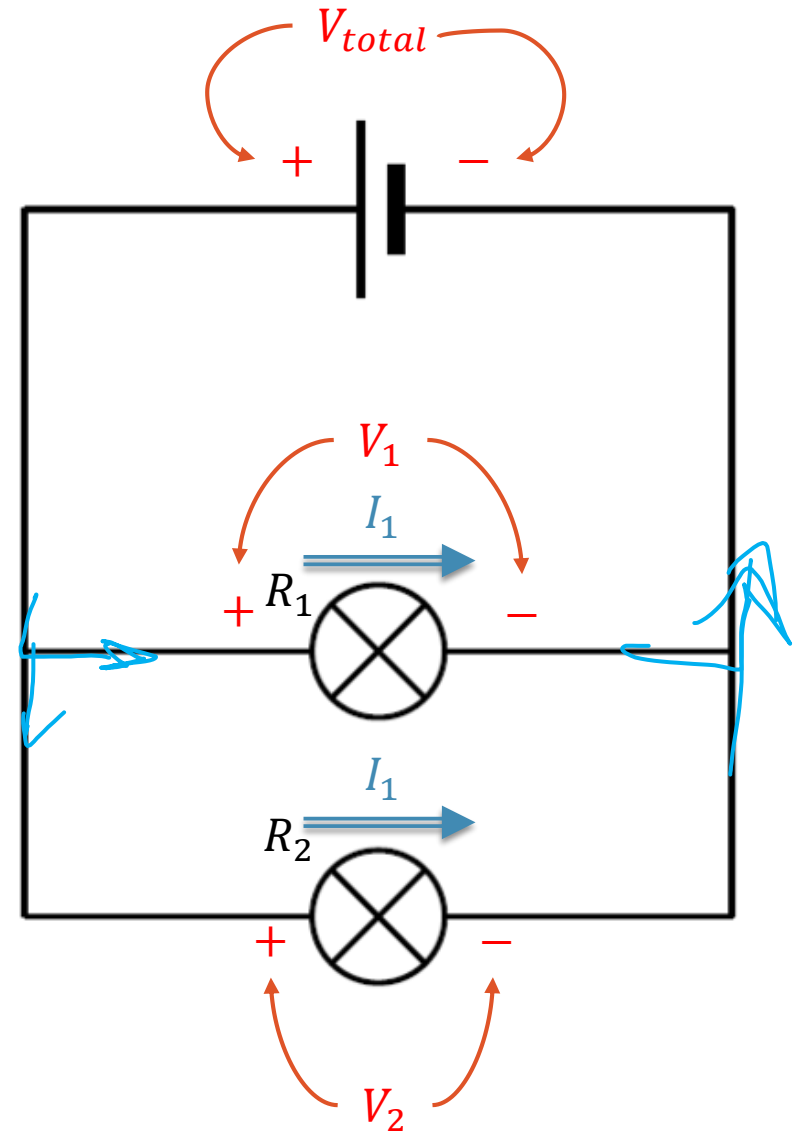
$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2}$$



# Simplifying a Parallel Circuit

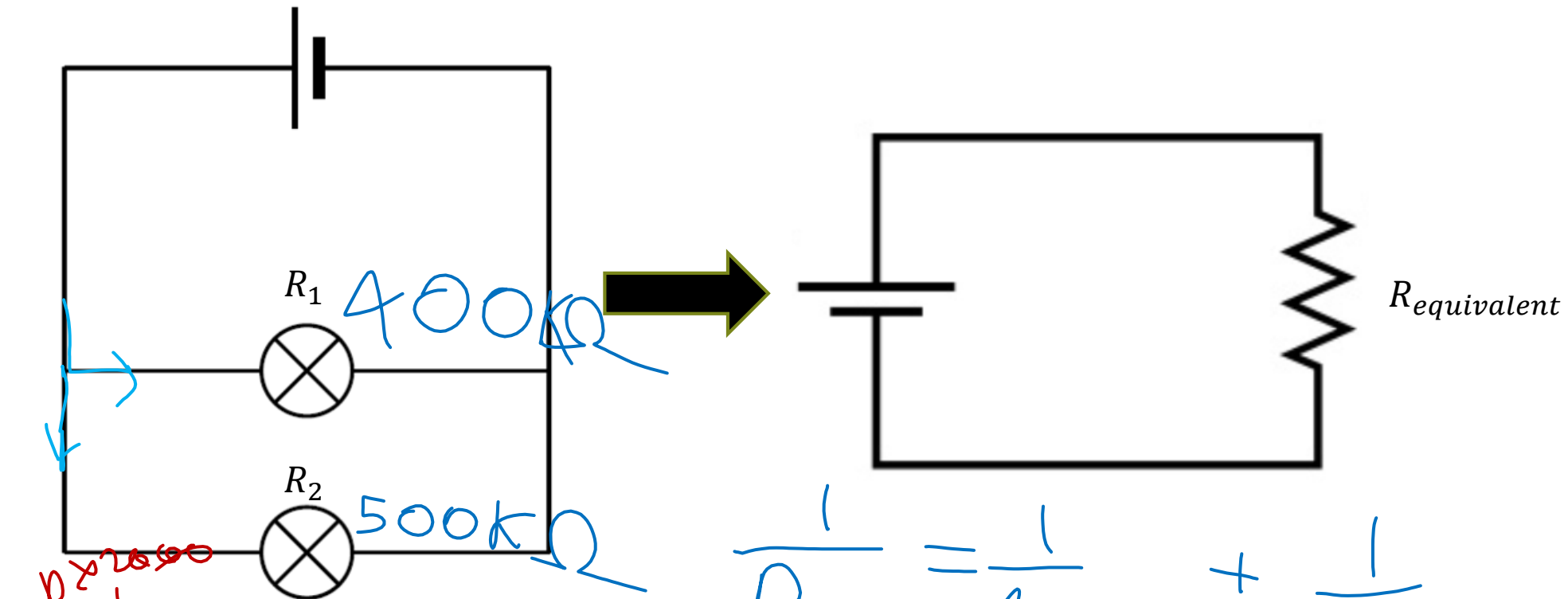

$$\frac{1}{R_T} = \frac{1}{2000} + \frac{1}{2000}$$

$$2000 = 2 R_T$$

$$R_T = 2000/2 = 1000 \Omega$$

$$\frac{1}{R_T} = \frac{1}{400} + \frac{1}{500}$$

$$\frac{1}{R_T} = \frac{5}{2000} + \frac{4}{2000} = \frac{9}{2000}$$

# Understanding the difference between Series and Parallel

## Series

- Voltage adds
- Constant current
- Resistance adds



- Think of water flowing through a hose
  - Water passing through one point needs to pass all points (constant current)
  - The longer the hose the more resistance (resistance adds)

## Parallel

- Voltage constant
- Current splits
- Resistance lessens



- Think of water flowing through a hose that splits into two hoses
  - At the split, less water flows into each hose (current splits)
  - Adding more hoses in parallel decreases the resistance (resistance lessens)

# MORE SERIES AND PARALLEL CIRCUITS

---

Wheeler HS Fall 2019




# Basic Circuit

$$I_{eq} = \frac{V_{eq}}{R_{eq}} = \frac{12V}{100\Omega} = 0.12A$$

$$V = IR$$



Voltage	Current	Resistance
$V_1 = 12V$	$I_1 = 0.12A$	$R_1 = 100\Omega$
$V_{eq} = 12V$	$I_{eq} = 0.12A$	$R_{eq} = 100\Omega$

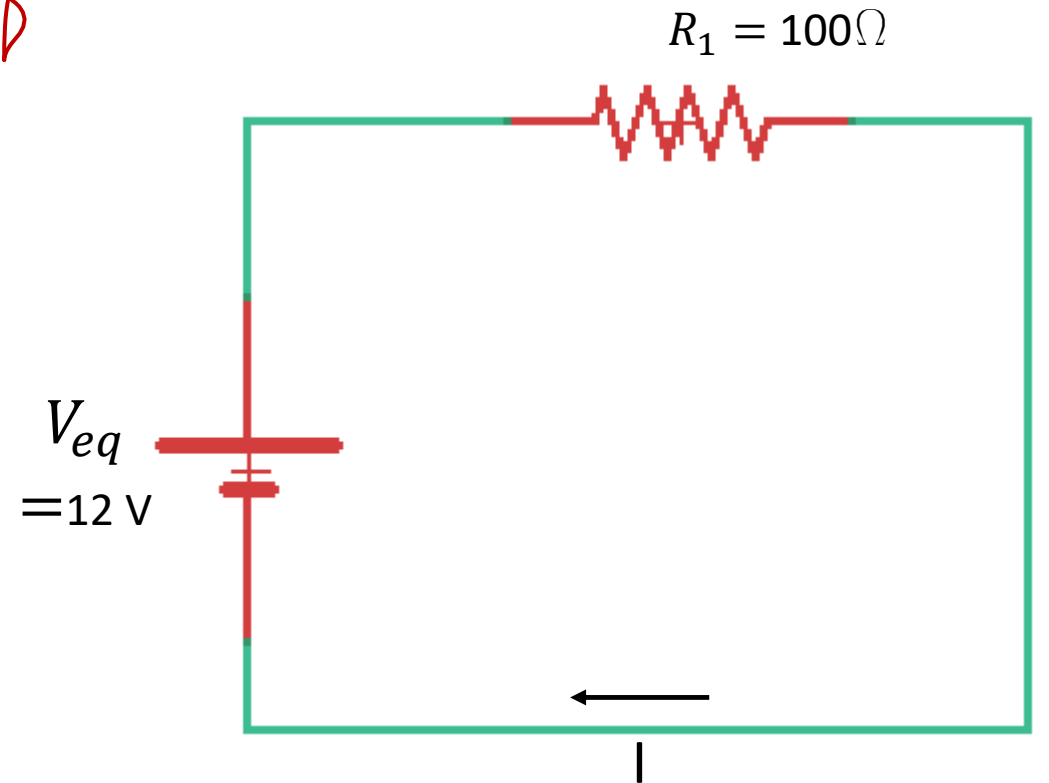

# Simplifying Series


Equivalent resistance for series circuits adds together

$$R_{total} = R_1 + R_2 + \dots$$

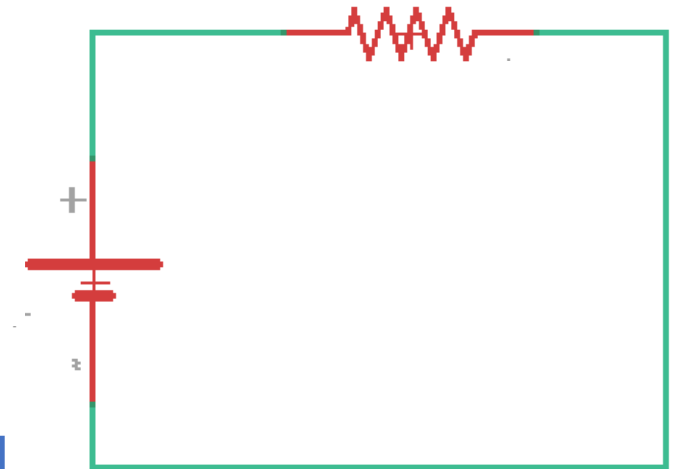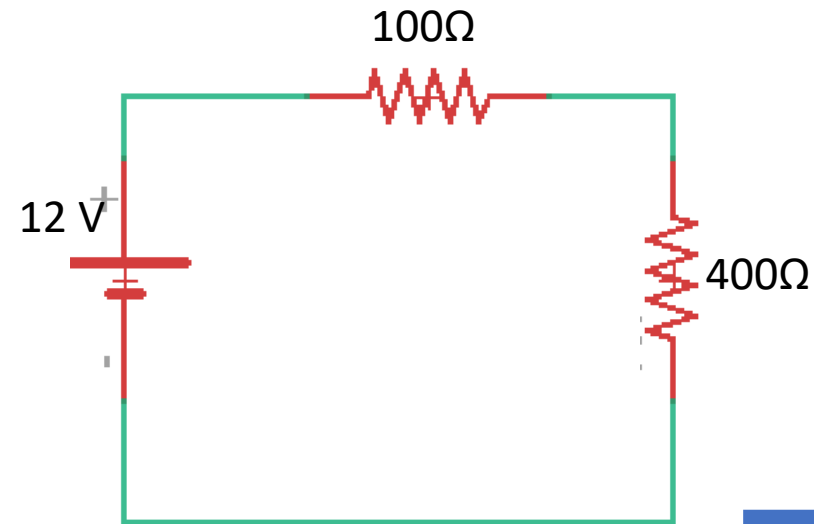

Voltage	Current	Resistance
$V_1 =$	$I_1 =$	$R_1 =$
$V_2 =$	$I_2 =$	$R_2 =$
$V_{eq} =$	$I_{eq} =$	$R_{eq} =$

# Another Series Example

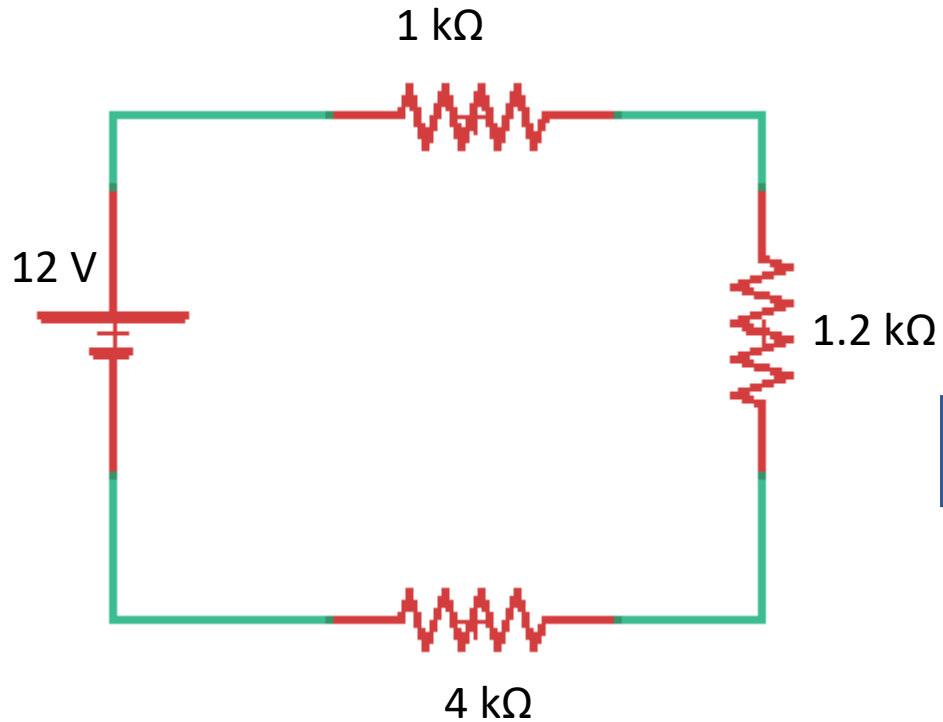

Find the equivalent resistance of this circuit



# Simplifying Parallel

Equivalent resistance for parallel circuits:

$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$
$$\frac{1}{R_T} = \frac{1}{250} + \frac{1}{250}$$
$$\frac{1}{R_T} = \frac{2}{250}$$




$$V_1 = 12V \quad I_1 = 0.048A \quad R_1 = 250\Omega$$

$$V_2 = 12V \quad I_2 = 0.048A \quad R_2 = 250\Omega$$

$$V_T = 12V \quad I_T = 0.096A \quad R_T = 125\Omega$$

# Another Parallel



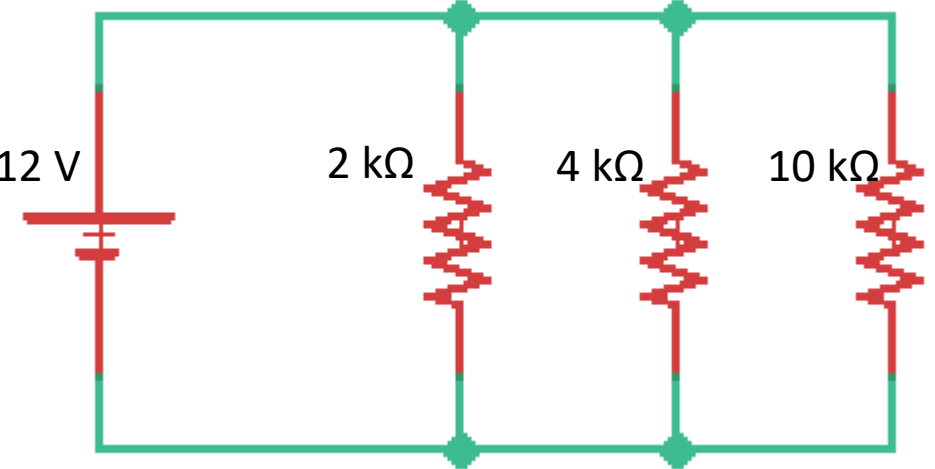


# Putting it together

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} \quad R_{23} \approx 133$$


$$\frac{1}{R_{23}} = \frac{1}{400} + \frac{1}{200} = \frac{3}{400}$$

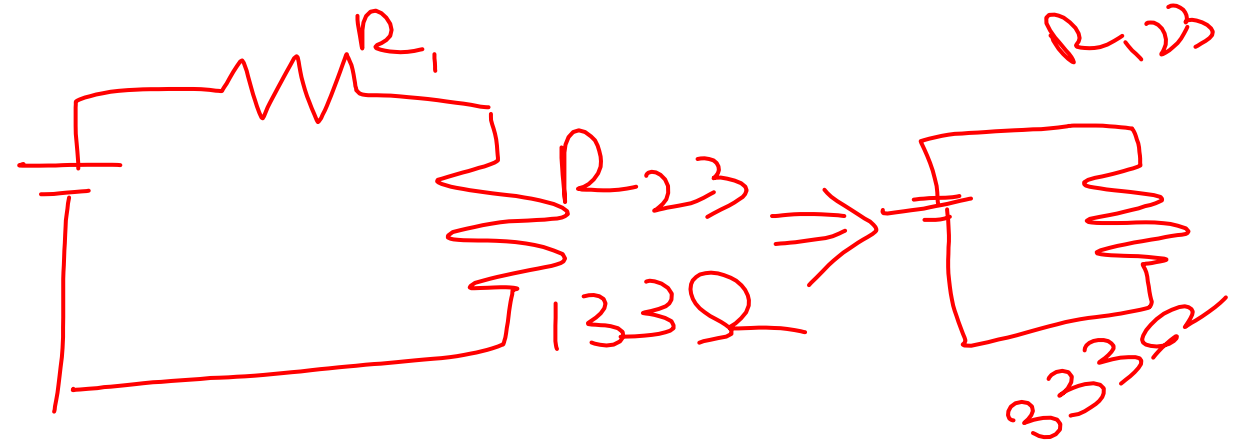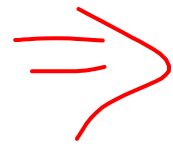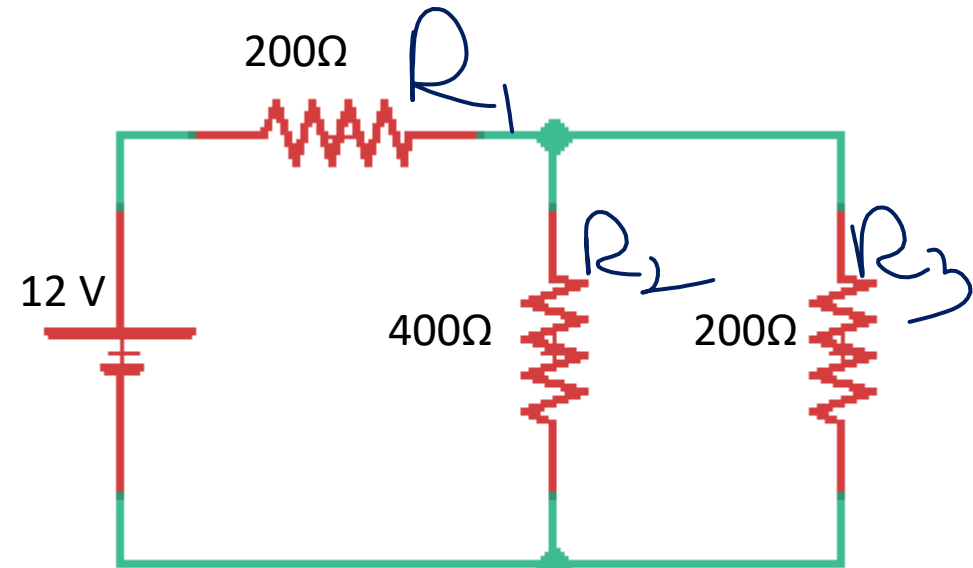Find the equivalent resistance of this circuit




$V_1 = 7.2V$ ,  $I_1 = 0.36A$ ,  $R_1 = 200\Omega$   
 $V_2 = 4.8V$ ,  $I_2 = 0.12A$ ,  $R_2 = 400\Omega$   
 $V_3 = 4.8V$ ,  $I_3 = 0.24A$ ,  $R_3 = 200\Omega$   
 $V_{23} = 4.8V$ ,  $I_{23} = 0.36A$ ,  $R_{23} = 133\Omega$   
 $V_T = 12V$ ,  $I_T = 0.36A$ ,  $R_T = 333\Omega$

# More!

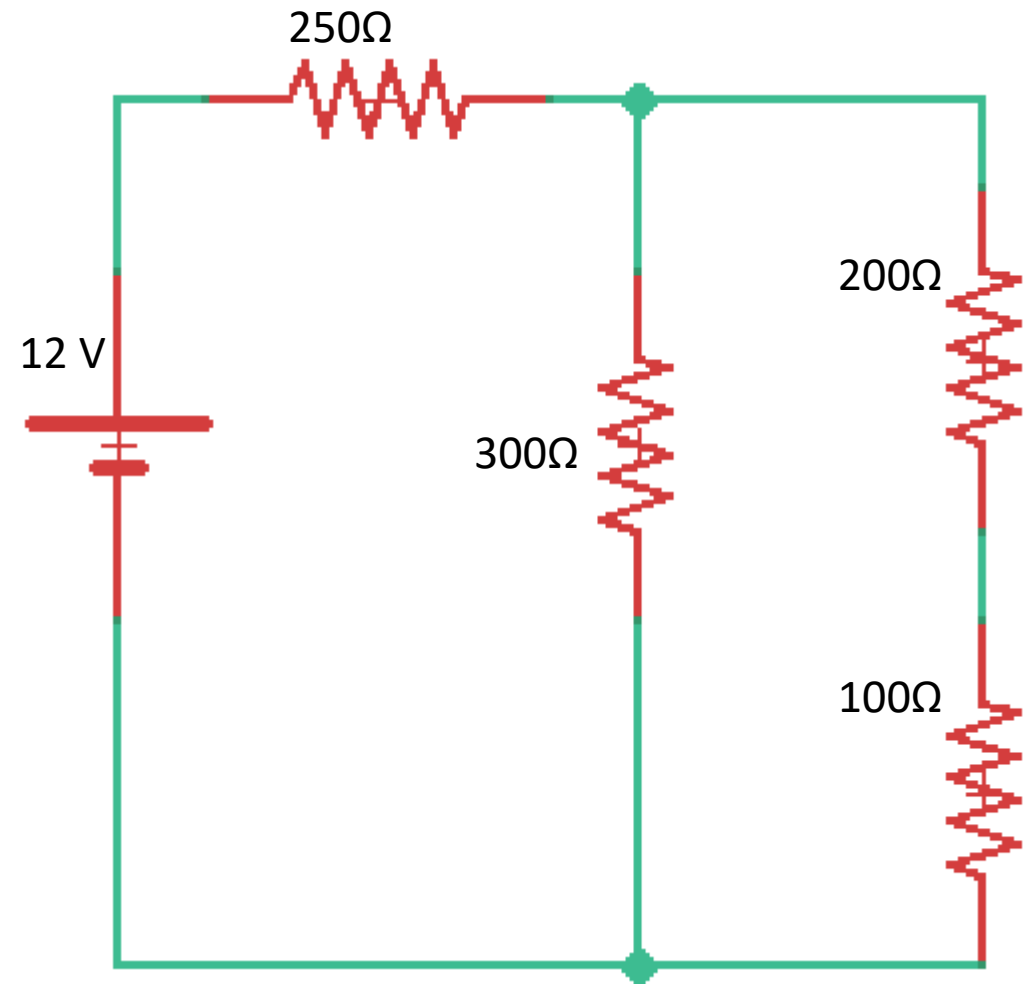

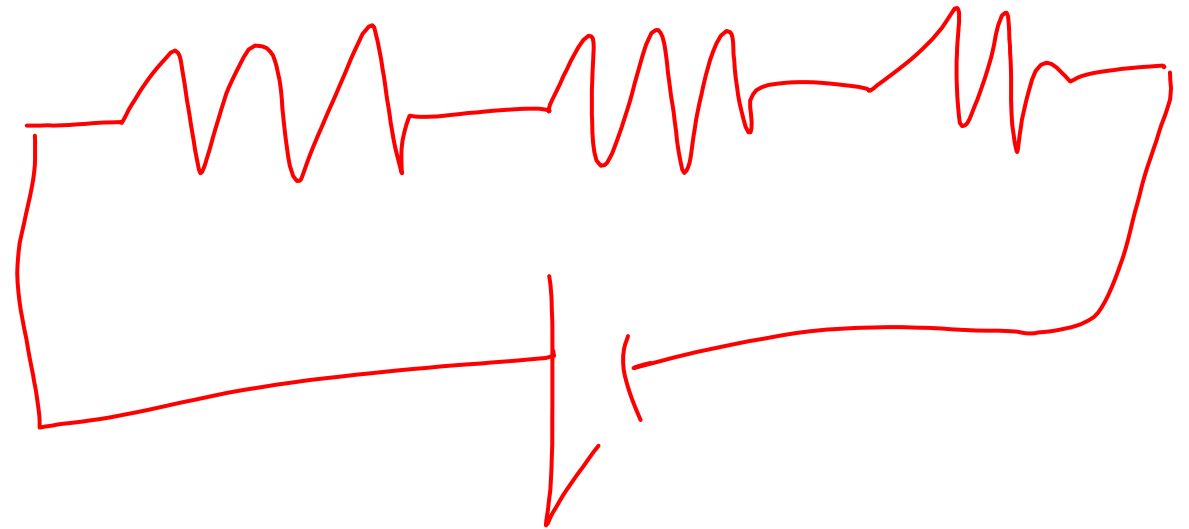Find the equivalent resistance of this circuit



v

# Closing

- You did it! You graduated High School and are now entering the corporate workforce doing what you do best: being a resistor. You (a resistor) wish to join a circuit with a good culture/benefits/dental-plan/etc., but are undecided on whether to join a circuit in parallel or in series. From a safety standpoint, do you think you should join a circuit in series or in parallel and why?