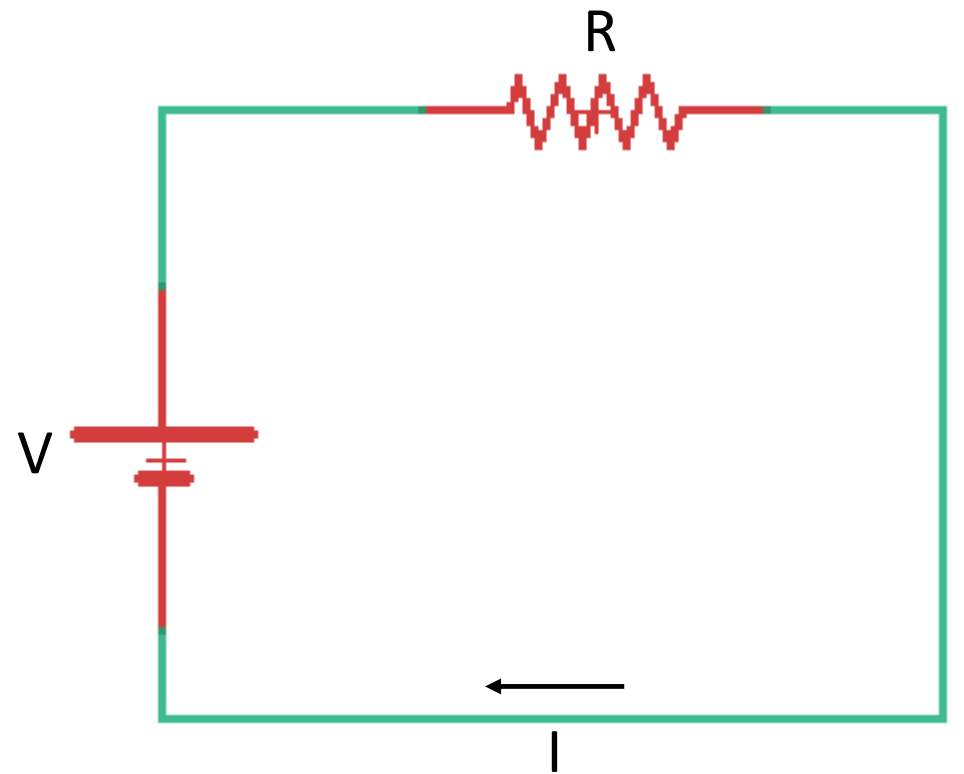


# More Series and Parallel Circuits

Wheeler HS Fall 2018

# Basic Circuit



$$V = IR$$




# Simplifying Series

Equivalent resistance for series circuits adds together

$$R_{total} = R_1 + R_2 + \dots$$

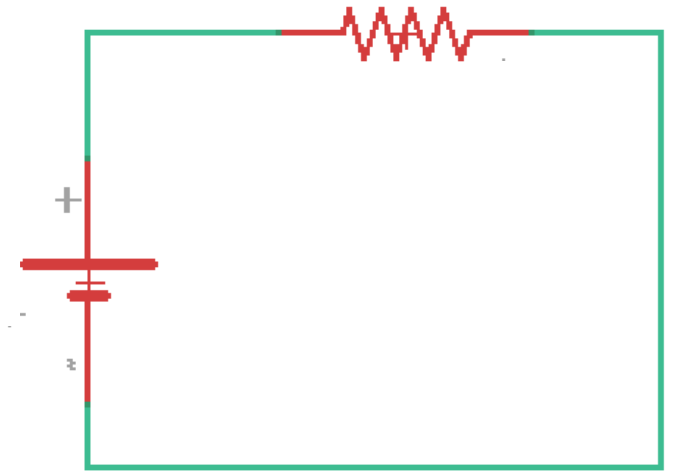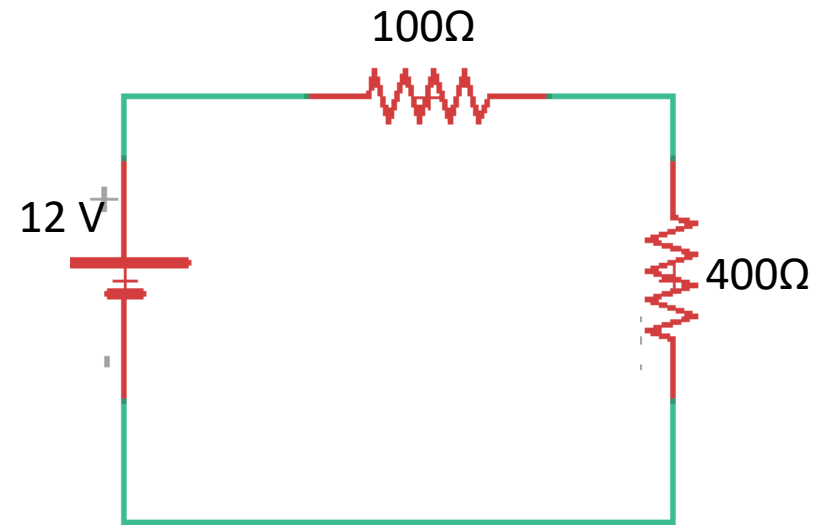



# Another Series Example

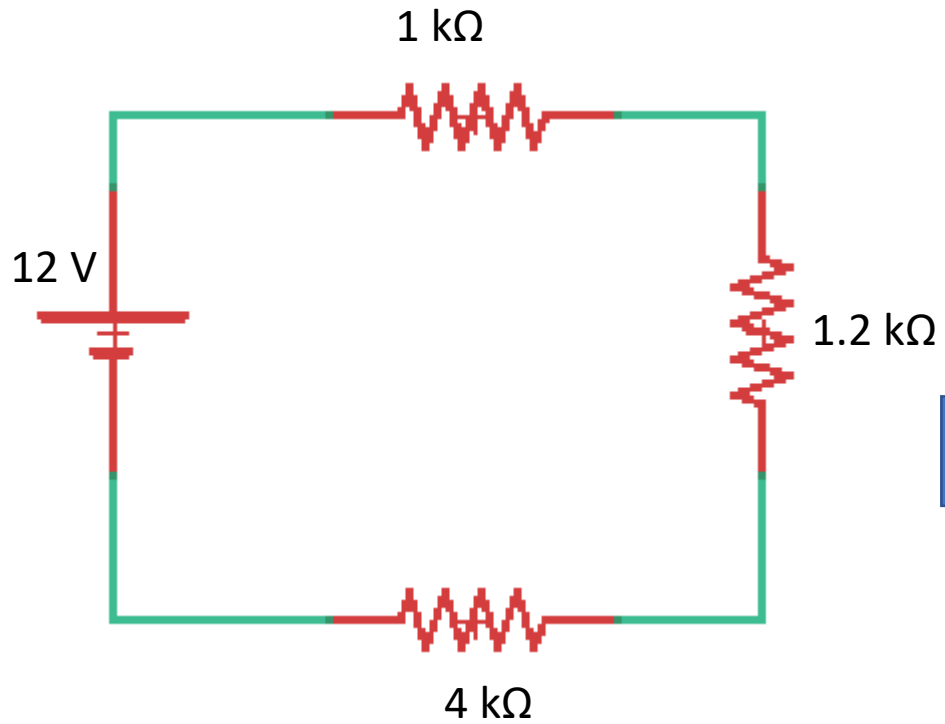

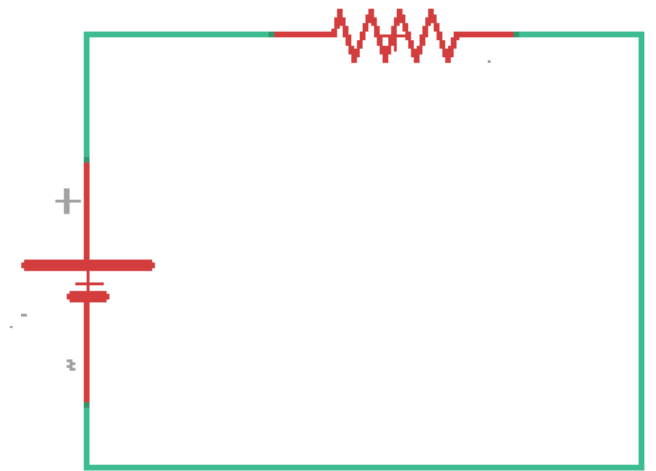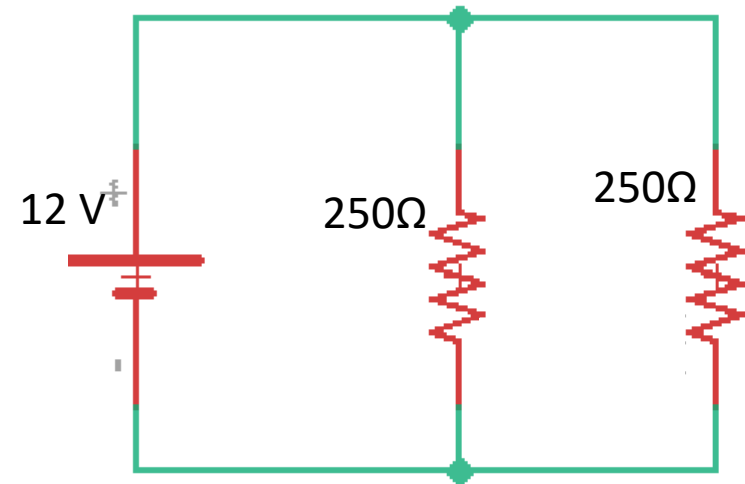
# Simplifying Parallel

Equivalent resistance for parallel circuits:


$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$



# Another Parallel

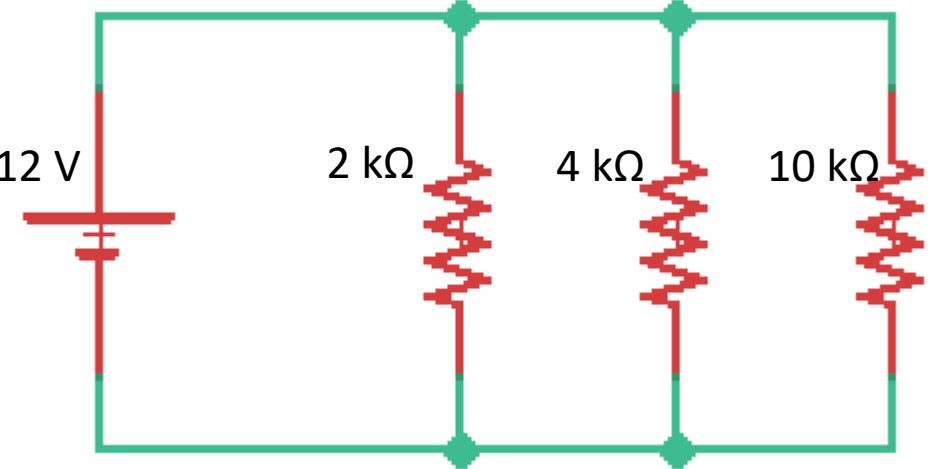

# Putting it together

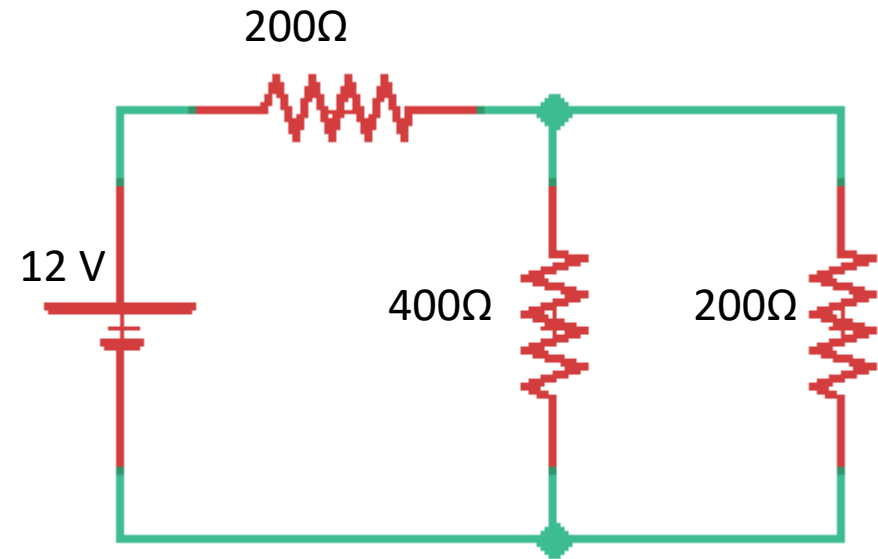

# More!

