

More Series and Parallel Circuits


Wheeler HS Fall 2018

Basic Circuit

$$V = IR$$

$$I = \frac{V}{R} = \frac{9V}{100\Omega}$$


$$I = 0.09 A$$

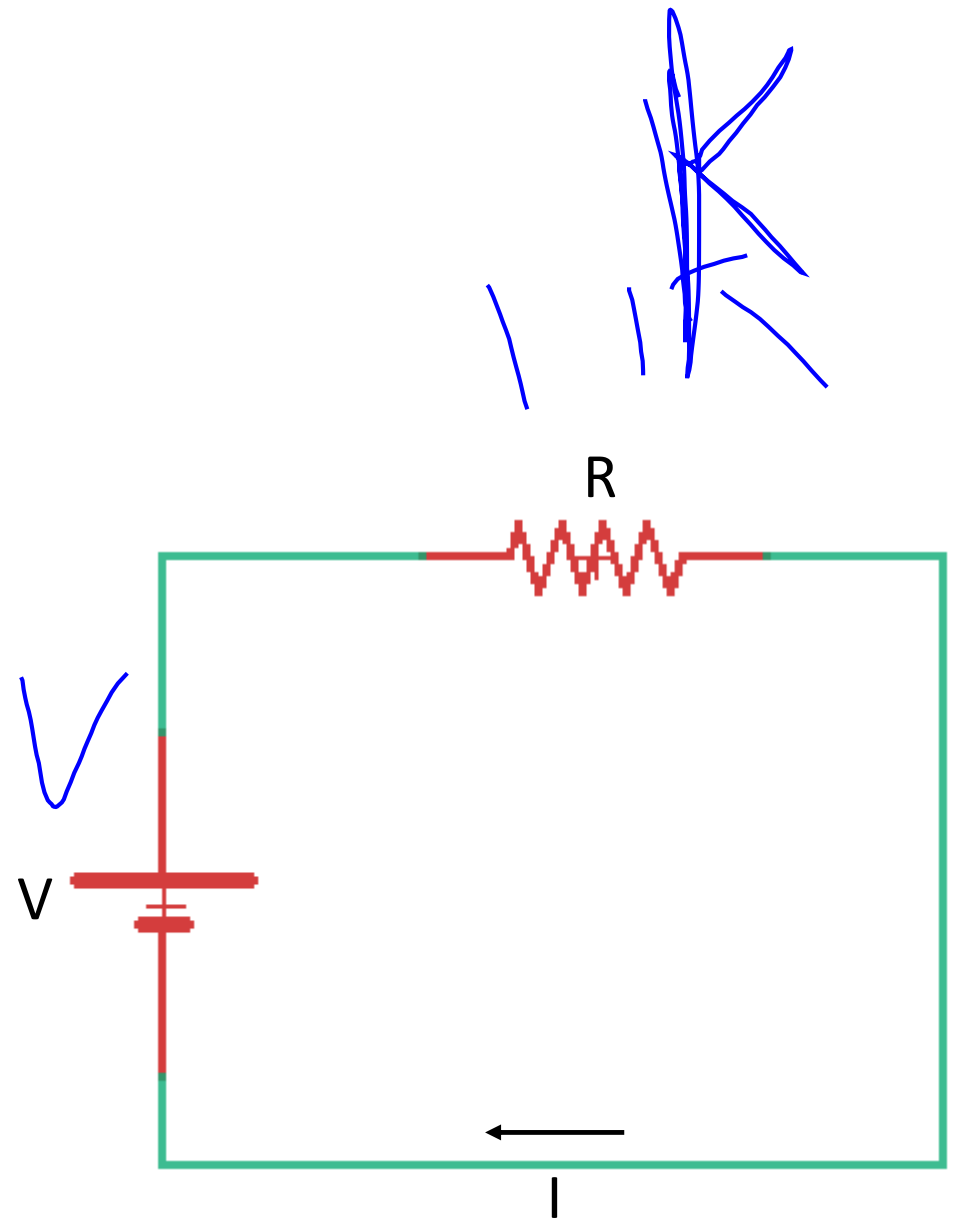


Simplifying Series

Equivalent resistance for series circuits adds together

$$R_{total} = R_1 + R_2 + \dots$$


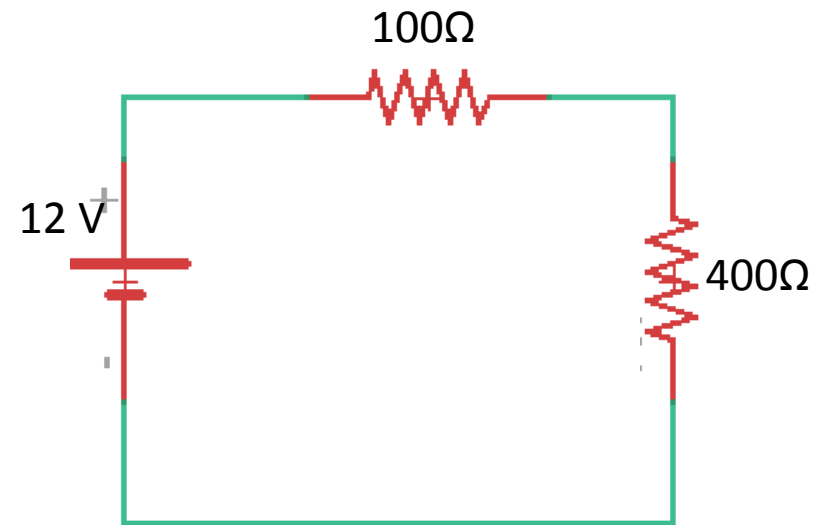


Handwritten blue text: $100 + 400$

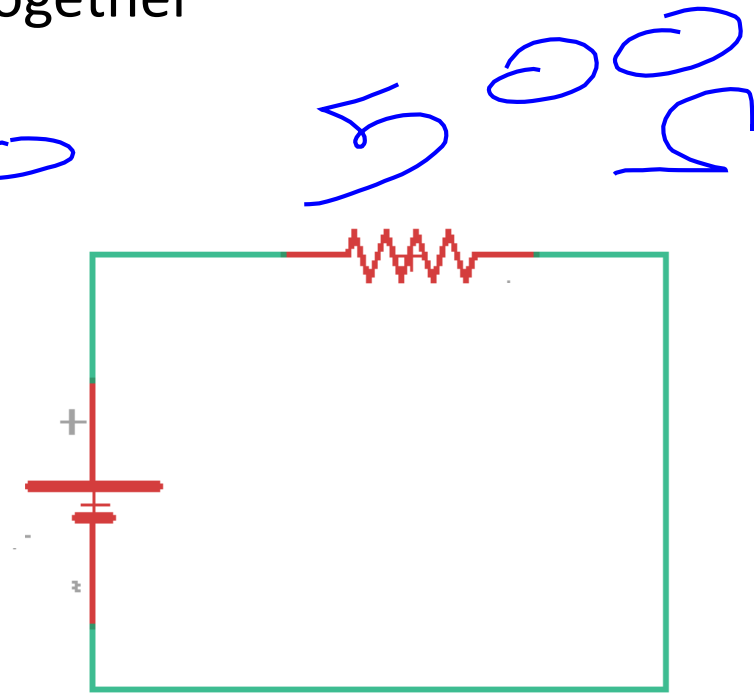

Another Series Example

$1k + 1.2k + 4k$

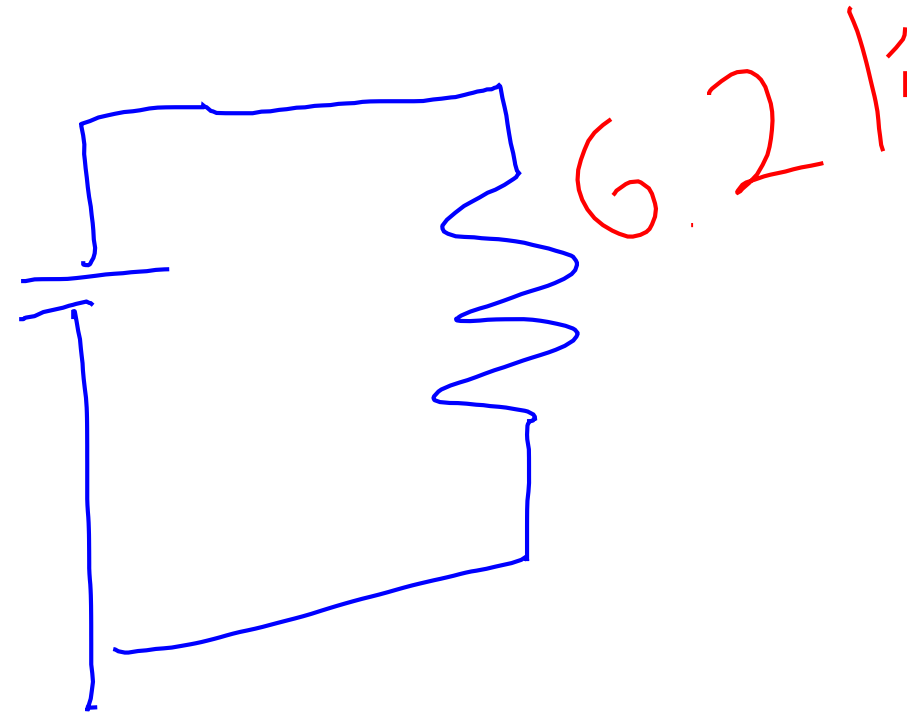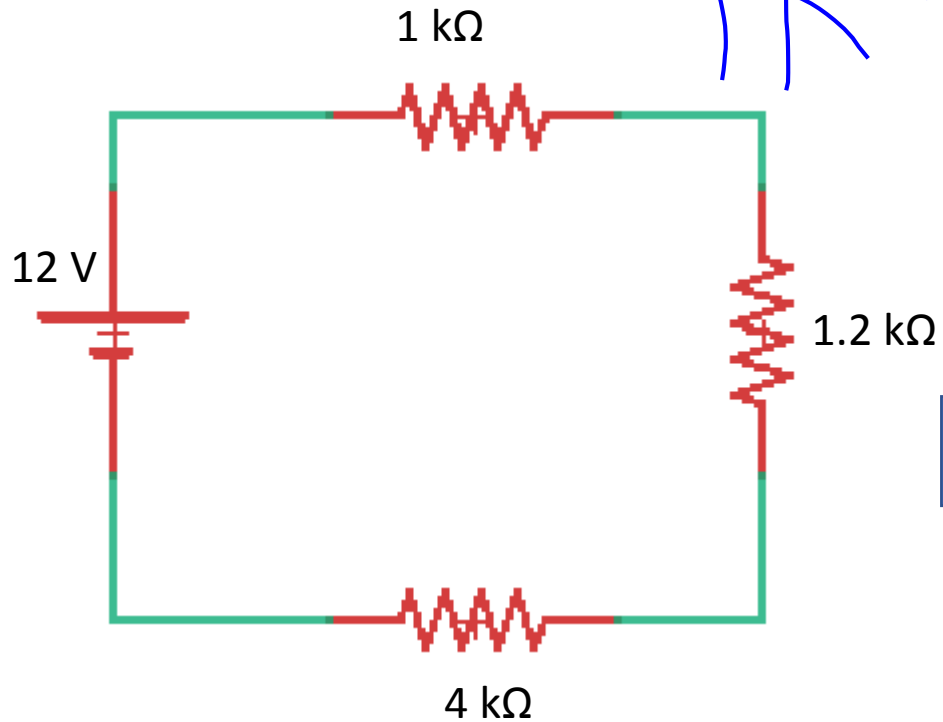



$6.2k = 6200\Omega$

Simplifying Parallel

Equivalent resistance for parallel circuits:

$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$
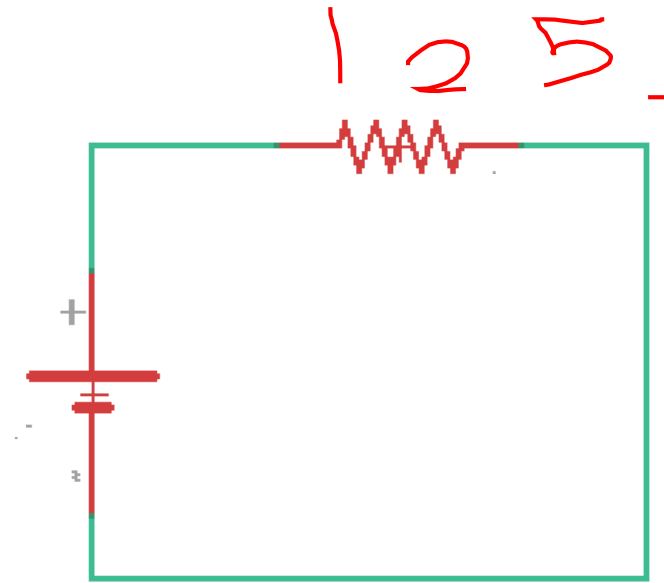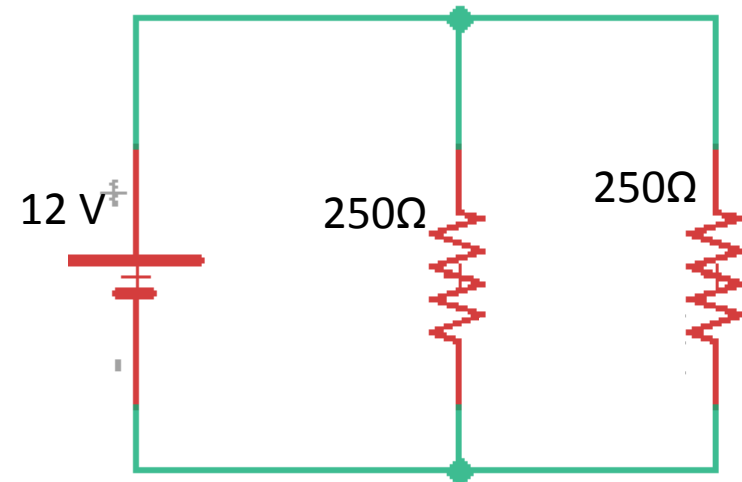
$$\frac{1}{R_T} = \frac{1}{125}$$
$$\frac{1}{R_T} = \frac{1}{250}$$
$$125 \Omega$$



$$\frac{1}{R_T} = \frac{1}{250} + \frac{1}{250} = \frac{1}{125}$$


Another Parallel

$$\frac{1}{R_T} = \frac{1}{2000} + \frac{1}{4000} + \frac{1}{10000}$$



$$\frac{1}{R_T} = 0.00175$$

$$R_T = 571.428571$$

$$R_T = 571 \Omega$$

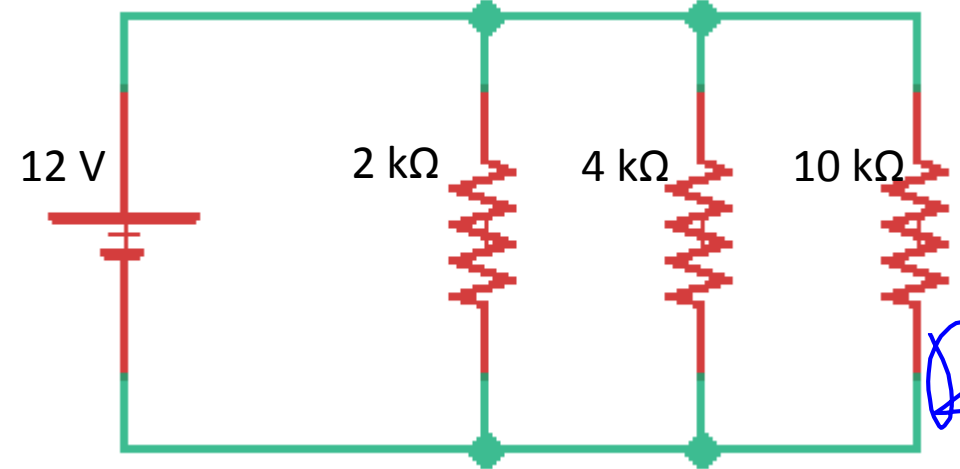


Putting it together

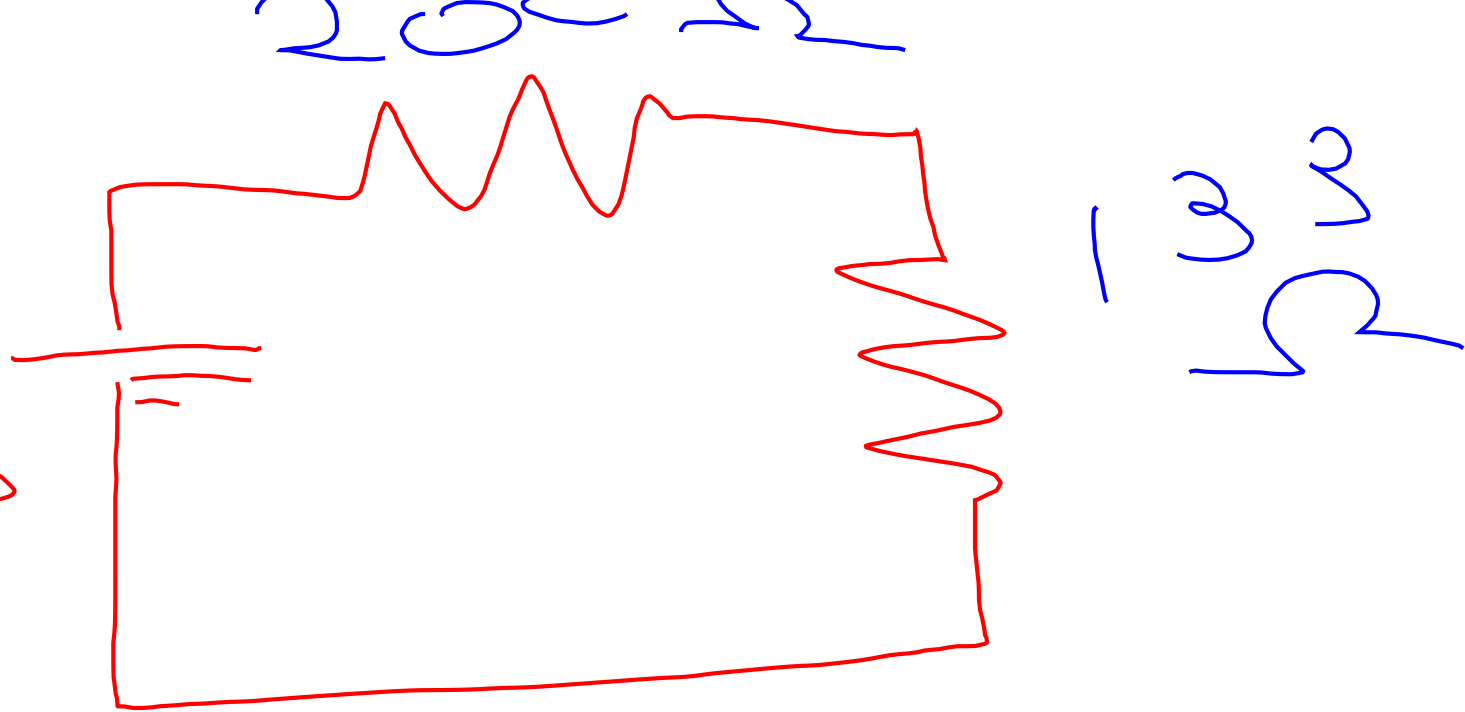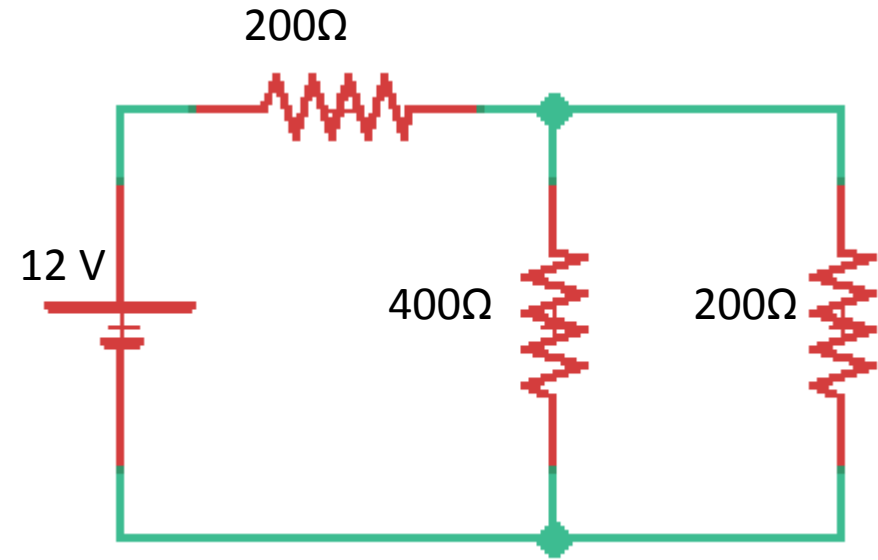

$$\frac{1}{R_T} = \frac{1}{200} + \frac{1}{400} + \frac{1}{200}$$

$$R_T = 100 \Omega$$

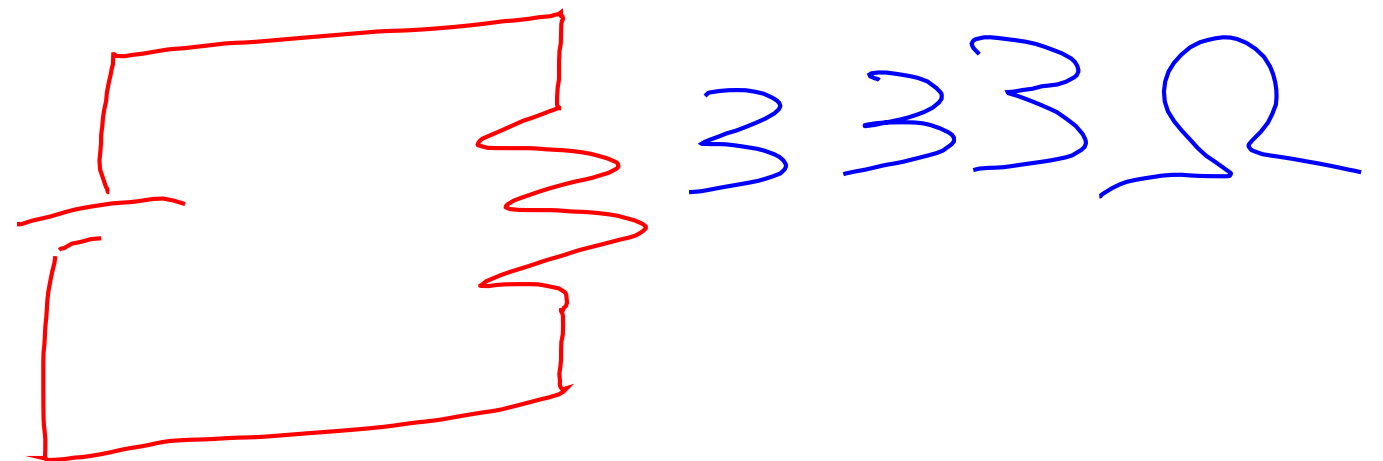

More!

